



SPI

(serial Peripheral Interface)

CMP1030 project 2021 _ Team #3

Member Name	ID	Sec	BN
أأمد صبري عبد الراضف أأمد	9202119	1	4
سماء أازم مأمء عبد اللطف	9202660	1	32
مأموء رضا سفء عبد العزفز	9203399	2	20
مأموء أأمد مأمء عطفة	9203543	2	26

Table of contents

The design process of each module & simulation results

Master Module **3**

Master's Test bench Module	9
Slave Module	12
Slave's Test bench Module	17
Simulation Results	22

Master Module

Parameters

a) Input :

- i) Clk (1 bit).
- ii) Reset (1 bit).
- iii) Start (1 bit).
- iv) MISO (1 bit).
- v) slaveSelect (2 bits).
- vi) masterDataToSend (8 bits).

b) Output :

- i) SCLK (1 bit).
- ii) CS (3 bits).
- iii) MOSI (1 bit).
- iv) masterDataReceived (8 bits).

•Master Design

- How does Master work ?

- Master module is built using “**Counter Circuit**”, which acts as:

1) Index to Data Sent & Data Received to determine which bit will be sent or received.

2) Stopping condition to Data Transmission process, After **8**

SCLK Cycles, Counter will be **8** then will terminate Transmission of Data.

How does Master generate outputs?

- Master module generates 4 outputs using Counter and Inputs according to the following Logic:

1) **Start_Signal** (internal reg)

Using **Start** signal (input), we generate Start_Signal that **Store** signal & **Begin** Data Transmission until all Data are shifted or sampled then **Stop** Transmission.

```
// using Counter to determine the bit which will be transmitted
always @(*)
begin
    if (start == 1 || (Counter > 0 && Counter < 8))
        //if((start == 1 && Counter == 0) || Counter < 8 )
        begin
            Start_Signal <= 1;
        end
    else
        begin
            Start_Signal <= 0;
            Counter = 0;
        end
end
```

2) SCLK

Using internal signal Start_Signal , We Generate **SCLK**,
When Start_Signal is High “1”, **SCLK** synchronized with **CLK**
When Start_Signal is Low “0”, **SCLK** is off “0”

```
// Generate SCLK from CLk  
assign SCLK = (Start_Signal)? clk : 0;
```

3) CS

Using **selectSlave & Start_Signal** input , we can determine
which slave will master **Send** or **Receive** from.

```
// Determine CS to send from SelectSlave  
assign CS = (Start_Signal == 0)? 3'b111:  
            (slaveSelect == 0)? 3'b011:  
            (slaveSelect == 1)? 3'b101:  
            (slaveSelect == 2)? 3'b110:3'b111;
```

4) MOSI

Using **SCLK** which is the cLock that outputs synchronized with,
On **Posedge**↑, we shift out **MasterDataToSend** to **MOSI** bit by
bit using Counter.

```
always @(posedge SCLK,posedge reset)
begin
    if(reset)
        begin
            Counter <= 0;
            masterDataReceived = 0;
        end
    else
        begin
            if(Counter<8)
            begin
                MOSI <= masterDataToSend[Counter];
                //Counter <= Counter_next;
            end
            else
            begin
                Counter = 0;
            end
        end
    end
end
```

5) MasterDataReceived

On **Negedge** ↓ ,We receive Data send by slave throught **MISO** & store it in **MasterDataReceived** bit by bit using counter.

```
always @(negedge SCLK,posedge reset)
begin
    if(reset)
        begin
            Counter <= 0;
        end
    else
        begin
            if(Counter<8)
            begin
                masterDataReceived [Counter] <= MISO;
                Counter <= Counter_next;
            end
            else
            begin
                Counter = 0;
            end
        end
    end
end
```


Master Test Banch

The data used to check the master:

Input data:

- *Clock(clk)*
- *Start*
- *Reset*
- *Miso*
- *Salve select of width(2)*
- *Master data to salve of width(8)*

Output data :

- *Sclk*
- *Mosi*
- *Cs of width(3)*
- *Master data received of width(8)*

Storage elements:

- *MOSI of width (8)*
- *MISO of width (8)*
- *testcase_masterData (array of 8 elements every element of width 8)*
- *testcase_salveData (array of 8 elements every element of width 8)*

the processes of the test:

1. *the clock will be changed every 10 units of time by using always block*
2. *using the initial block to initialize some data like*
(clock,start,reset, testcase_masterData,
testcase_salveData ,SalveSelect,)

the logic:

*Using for loop to initialize the data like (**Master data to solve and Miso**) and the processes of initializing the first variable by using a temporary parameter (**testcase_masterData**).*

*After initializing the data, we fill the testing data, we fill the parameter (**MOSI**) from the output (**Mosi**) in each period and after eight iterations, the variable (**MOSI**) will be completely filled.*

*In the end of each iteration we check the data by using if condition and if the data is correct, it displays “**successful**” and if the data is incorrect, it displays “**failed**” and the check will be between the (**testcase_solveData&&MasterDataReceived**) and(**MOSI&&MasterDataToSolve**).*

Slave Module

Parameters

a) Input :

- i) SClk (1 bit).
- ii) reset (1 bit).
- iii) CS (1 bit).
- iv) MOSI (1 bit).
- v) slaveDataToSend (8 bits)

b) Output :

- i) MISO (1 bit).
- ii) slaveDataReceived (8 bits).

Slave Design

1) Count:

-The algorithm of setting the data in slaveDataReceived from MOSI is the same as setting the data in masterDataReceived from MISO , it is done by replacing bit by bit using data "Count" which increments with each cycle.

-It is important to add this part of code to set Count to zero again if we finish the 8 cycles, which we determined before to perform the receiving and sending operations.

```
count=count+1;  
if(count==4'b1000)  
begin  
    count=4'b0000;  
end
```

```
count_2=count_2+1;  
if(count_2==4'b1000)  
begin  
    count_2=4'b0000;  
end
```

2) Reset:

if reset=1, we reset the data of slave , Count , or slaveDataReceived and set MISO with "z"

```
if(reset==1'b1)  
begin  
    slaveDataReceived<=8'b00000000;  
    count<=4'b0000;  
    MISO<=1'bz;  
end
```

3) CS:

1-if CS=1,no receiving or sending is done through the slave , we just set the output MISO of this slave to "z" to prevent this slave to overwrite in MISO , it is important if there are many slaves connected with the master , so we allow the master to receive the data from the slave which it targets and sets this slave's CS with 0.

```
else if (CS==1)
begin
    MISO<=1'bz;
end
```

2-If CS=0, then both operations work

4) SCLK:

•If CS=0 and for each cycle:

1-at the **negative edge** of SCLK , we set the data coming from the master (MOSI) to the bit (which has the turn in this cycle) of the slaveDataReceived.

```
always @( negedge SCLK ,posedge reset)
begin
  if(reset==1'b1)
    begin
      slaveDataReceived<=8'b00000000;
      count<=4'b0000;
      MISO<=1'bz;
    end
  else if(CS==0)
    begin
      if(count!=4'b1000)
        begin
          slaveDataReceived[count]=MOSI;
          count=count+1;
          if(count==4'b1000)
            begin
              count=4'b0000;
            end
        end
      end
    end
end
```

2-at the **positive edge** of SCLK, we set the bit (which also has the turn in this cycle) of the slaveDataToSend to the MISO.

```
always @( posedge SCLK )
begin
    if (CS==0 && reset==1'b0)
        begin
            if (count_2!=4'b1000)
                begin
                    MISO=slaveDataToSend[count_2];
                    count_2=count_2+1;
                    if (count_2==4'b1000)
                        begin
                            count_2=4'b0000;
                        end
                end
            end
        end
    else if (CS==1)
        begin
            MISO<=1'bz;
        end
    end
end
```


Slave Test Banch

[I]Declaring variables ,used Regs & Wires

```
1 module Slave_TB ();
2
3 reg reset;
4 reg [7:0] slaveDataToSend;//input
5 wire [7:0] slaveDataReceived;//output
6 reg SCLK;
7 reg CS;
8 reg MOSI;
9 wire MISO;
10 wire [7:0] testcase_slaveData [1:/*TESTCASECOUNT*/4];
11 wire [7:0] testcase_masterData [1:/*TESTCASECOUNT*/4];
12 integer i,j;
13 reg [7:0] masterDataReceived;
14 localparam PERIOD = 10;
15 Slave UUT_S(
16     reset,
17     slaveDataToSend, slaveDataReceived,
18     SCLK, CS, MOSI, MISO
19 );
```

A- Regs

- 1) Reset
- 2) SCLK: slave simulation Clock
- 3) CS: slave ship select
- 4) MOSI: Master Output slave input
- 5) SlaveDataToSend (8 bits): Data stored in Slave to be sent to master [TestCase]

6) MasterDataReceived (8 bits): Data data send from slave and received in master
[TestCase]

B- Wires:

- 1) MISO
- 2) Slave Data Received (8 bits) (Module output, Net data recieved)
- 3) testcase_slaveData (8 bits) ,array of 4 Testcases for slave data
- 4) testcase_masterData (8 bits) ,array of 4 Testcases for master data

C- Variables

- 1) i -> integer to loop 4 times to test the 4 testcases
- 2) j -> for inner loop , which will be discussed later
- 3) UUT_S -> Slave module instance
- 4) LocalParameter PERIOD -> timeperiod of full SCLK cycle

[II]Setting up SCLK

In this test bench only, we assume that SCLK is synchronous, unlike real deal in the Development module, so in testing only the slave module, we assume that only one slave is sending to and receiving from one master (SCLK = ~Master's CLK)

```
always #(PERIOD/2) SCLK = ~SCLK;
```

[III]Setting up Test cases

Here we have chosen 4 test cases for verifying successful transmission to and from slave module

```
27 assign testcase_slaveData[1] = 8'b00000000;//data send from slave and received in master
28 assign testcase_slaveData[2] = 8'b11111111;
29 assign testcase_slaveData[3] = 8'b10000011;
30 assign testcase_slaveData[4] = 8'b10011010;
31
32 assign testcase_masterData[1] = 8'b00000000;//data send from master and received in slave
33 assign testcase_masterData[2] = 8'b11111111;
34 assign testcase_masterData[3] = 8'b00100000;
35 assign testcase_masterData[4] = 8'b01111111;
```

[IV] Ports Initialization

```
initial begin
    SCLK = 1;
    reset = 1;
    #PERIOD reset = 0;
    i=0;j=0;
    CS = 0;
```

[V] Testing logic

```
38 for(i = 1; i<=4;i=i+1)
39 begin
40
41     $display("Running test set %d", i);
42     slaveDataToSend=testcase_slaveData[i];
43     for(j = 0; j<8;j=j+1)
44     begin
45         #(PERIOD/2) MOSI = testcase_masterData[i][j];
46         #(PERIOD/2) masterDataReceived[j]=MISO;
47     end
48     if(slaveDataReceived == testcase_masterData[i]) $display("From Master to Slave : Success");
49     else begin
50         $display("From Master to Slave : Failure (Expected: %b, Received: %b)", testcase_masterData[i], slaveDataReceived);
51     end
52     if(masterDataReceived == testcase_slaveData[i]) $display("From Slave to Master : Success");
53     else begin
54         $display("From Slave to Master : Failure (Expected: %b, Received: %b)", testcase_slaveData[i], masterDataReceived);
55     end
56 end
57 $finish;
58 end
59
60
61 endmodule
```

#1: loop on 4 test cases from i = 0 to 4

#2: in each loop:

- displays ID of test case

- executes inner loop of j from 0 to 7(chosen 8 loops for 8 bits, 0 to 7

for significance of ports)

->to send and receive from slave, in each inner loop:

- assigns at +ve edge the j^{th} bit to MOSI
- assigns at -ve edge the MISO bit to j^{th} bit of masterDataReceived

- After inner loop finish, the test data should be transmitted and received successfully

, being a self-checking testbench , it does 2 checks:

```
•#1 :  
  
if  
(slaveDataReceived == testcase_masterData[i])
```

>meaning: if Module Net output data received by slave is identical to current sent masterdata testcase

```
•#2 :  
  
if(masterDataReceived == testcase_slaveData[i])
```

>meaning: if Module Net output data received by master is identical to current sent slavedata testcase

- At the end, whenever a check is true: it displays

"From Master to Slave : Success" in #1

"From Slave to Master : Success" in #2



If false, it displays that it was a failure & displays both the expected output & the wrong one

Simulation Results

The output and the wave form

  
#1 Master TB

```
Transcript
# TestCase      1
# successful Send
# successful Receive
# TestCase      2
# successful Send
# successful Receive
# TestCase      3
# successful Send
# successful Receive
# TestCase      4
# successful Send
# successful Receive
# TestCase      5
# successful Send
# successful Receive
# TestCase      6
# successful Send
# successful Receive
# TestCase      7
# successful Send
# successful Receive
# TestCase      8
# successful Send
# successful Receive
# SUCCESS: All      16 testcases have been successful
# ** Note: $finish    : D:/pdf/Engineering/SecondTerm/AdvancedLogicDesign/Master_tb.v(100)
# Time: 1955 ps Iteration: 0 Instance: /Master_tb
```


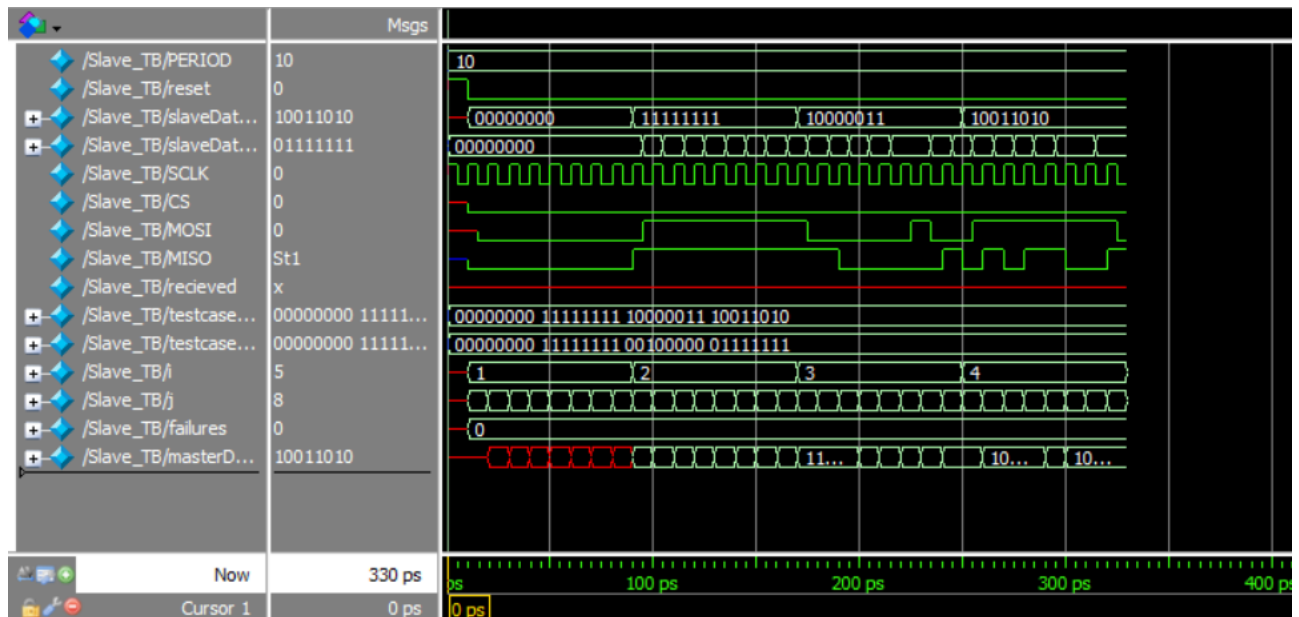
#2 Slave TB

```
# 5 compiles, 0 failed with no errors.
ModelSim> vsim {SPI Library.Slave_TB}
# vsim SPI Library.Slave_TB
# Start time: 14:43:46 on May 31,2021
# Loading SPI Library.Slave_TB
# Loading SPI Library.Slave
VSIM 2> run -all
# Running test set          1
# From Master to Slave : Success
# From Slave to Master : Success
# Running test set          2
# From Master to Slave : Success
# From Slave to Master : Success
# Running test set          3
# From Master to Slave : Success
# From Slave to Master : Success
# Running test set          4
# From Master to Slave : Success
# From Slave to Master : Success
# ** Note: $finish      : D:/2nd Term/Logic II/Project/Slave_TB.v(101)
#   Time: 330 ps  Iteration: 0  Instance: /Slave_TB
# 1
# Break in Module Slave_TB at D:/2nd Term/Logic II/Project/Slave_TB.v line 101
VSIM 3>
```



#3 Development TB

```
VSIM 4> run -all
# Running test set      1
# From Slave 0 to Master: Success
# From Master to Slave 0: Success
# From Slave 1 to Master: Success
# From Master to Slave 1: Success
# From Slave 2 to Master: Success
# From Master to Slave 2: Success
# Running test set      2
# From Slave 0 to Master: Success
# From Master to Slave 0: Success
# From Slave 1 to Master: Success
# From Master to Slave 1: Success
# From Slave 2 to Master: Success
# From Master to Slave 2: Success
# SUCCESS: All      12 testcases have been successful
# ** Note: $finish      : D:/2nd Term/Logic II/Project/DevelopmentTB.v(108)
#   Time: 2540 ps  Iteration: 0  Instance: /DevelopmentTB
# 1
# Break in Module DevelopmentTB at D:/2nd Term/Logic II/Project/DevelopmentTB.v line 108
VSIM 5>
```